
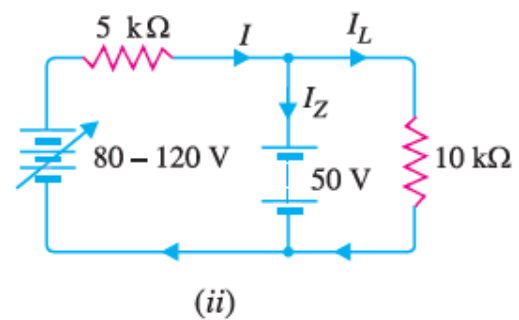


1. V_{in} is 40 V, R_1 is $50\ \Omega$, R_L is $100\ \Omega$ and the breakdown voltage of the zener diode 12V
 - (a) What is the voltage drop across the load resistance R_L ?
 - (b) Calculate the current through the load resistor R_L .
 - (c) What is the voltage drop across R_1 ?
 - (d) Calculate the current through R_1 .
 - (e) What is the current through the zener diode?

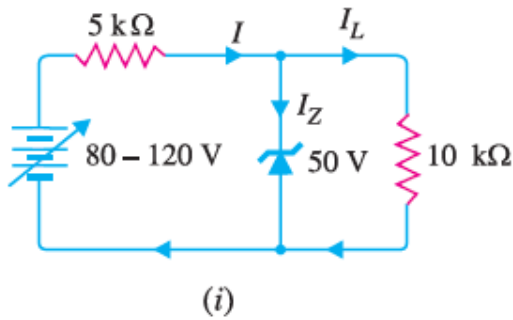2. For the circuit shown in Fig. 2 (i), find the maximum and minimum values of zener diode current.



3. The zener diode shown in Fig. 3 has $V_Z = 18\text{ V}$. The voltage across the load stays at 18 V as long as I_Z is maintained between 200 mA and 2 A. Find the value of series resistance R so that E_O remains 18 V while input voltage E_i is free to vary between 22 V to 28V.

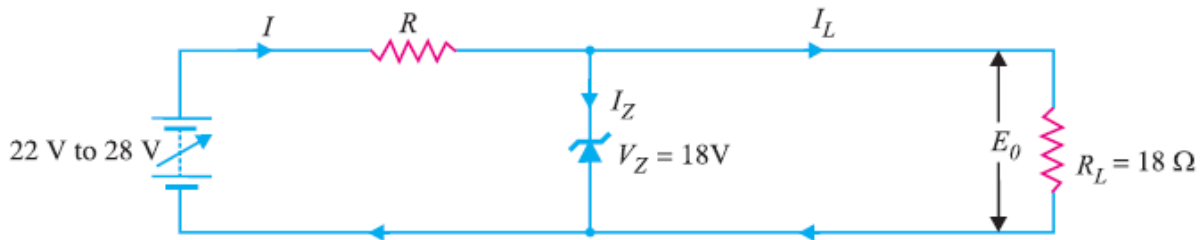


Fig. 3

4. The circuit of Fig. 6 uses two zener diodes, each rated at 15 V, 200 mA. If the circuit is connected to a 45-volt unregulated supply, determine : (i) The regulated output voltage (ii) The value of series resistance R .


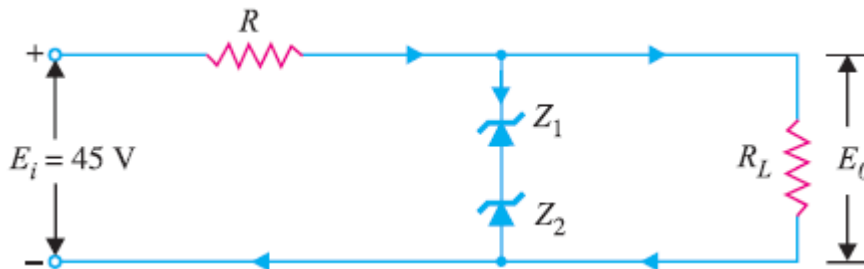



Fig. 4

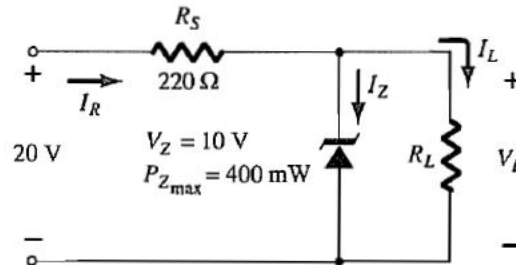- Determine V_L , I_L , I_Z , and I_R for the network Fig. 2.181 if $R_L = 180\ \Omega$.
- Repeat part (a) if $R_L = 470\ \Omega$.
- Determine the value of R_L that will establish maximum power conditions for the Zener diode.
- Determine the minimum value of R_L to ensure that the Zener diode is in the "on" state.



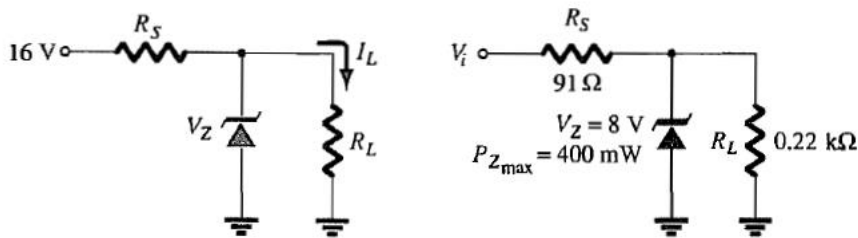5.

For the network of Fig. 2.183, determine the range of V_i that will maintain V_L at 8 V and not exceed the maximum power rating of the Zener diode.



6.

- (a) Design the network to maintain V_L at 12 V for a load variation (I_L) from 0 to 200 mA. That is, determine R_S and V_Z . (b) Determine P_{Zmax} for the Zener diode of part (a).