

FIELD EFFECT TRANSISTOR (FET)

PREPARED BY-

SADIA ENAM,

LECTURER, DEPT. OF IRE, BDU

SHORTHAND METHOD

If we specify V_{GS} to be one-half the pinch-off value V_P ,

$$\begin{aligned}I_D &= I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \\&= I_{DSS} \left(\frac{1 - V_P/2}{V_P} \right)^2 = I_{DSS} \left(1 - \frac{1}{2} \right)^2 = I_{DSS} (0.5)^2 \\&= I_{DSS} (0.25)\end{aligned}$$

and

$$I_D = \frac{I_{DSS}}{4} \Big|_{V_{GS}=V_P/2}$$

If we choose $I_D = I_{DSS}/2$

$$\begin{aligned}V_{GS} &= V_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}} \right) \\&= V_P \left(1 - \sqrt{\frac{I_{DSS}/2}{I_{DSS}}} \right) = V_P (1 - \sqrt{0.5}) = V_P (0.293)\end{aligned}$$

and

$$V_{GS} \cong 0.3V_P \Big|_{I_D=I_{DSS}/2}$$

V_{GS} Versus I_D Using Shockley's Equation

V_{GS}	I_D
0	I_{DSS}
$0.3V_P$	$I_{DSS}/2$
$0.5V_P$	$I_{DSS}/4$
V_P	0 mA

SHORTHAND METHOD

EXAMPLE 6.1 Sketch the transfer curve defined by $I_{DSS} = 12 \text{ mA}$ and $V_P = -6 \text{ V}$.

Solution: Two plot points are defined by

$$I_{DSS} = 12 \text{ mA} \quad \text{and} \quad V_{GS} = 0 \text{ V}$$


and

$$I_D = 0 \text{ mA} \quad \text{and} \quad V_{GS} = V_P$$


At $V_{GS} = V_P/2 = -6 \text{ V}/2 = -3 \text{ V}$ the drain current is determined by $I_D = I_{DSS}/4 = 12 \text{ mA}/4 = 3 \text{ mA}$. At $I_D = I_{DSS}/2 = 12 \text{ mA}/2 = 6 \text{ mA}$ the gate-to-source voltage is determined by $V_{GS} \cong 0.3V_P = 0.3(-6 \text{ V}) = -1.8 \text{ V}$. All four plot points are well defined on Fig. 6.18 with the complete transfer curve.

V_{GS} Versus I_D Using Shockley's Equation

V_{GS}	I_D
0	I_{DSS}
$0.3V_P$	$I_{DSS}/2$
$0.5V_P$	$I_{DSS}/4$
V_P	0 mA

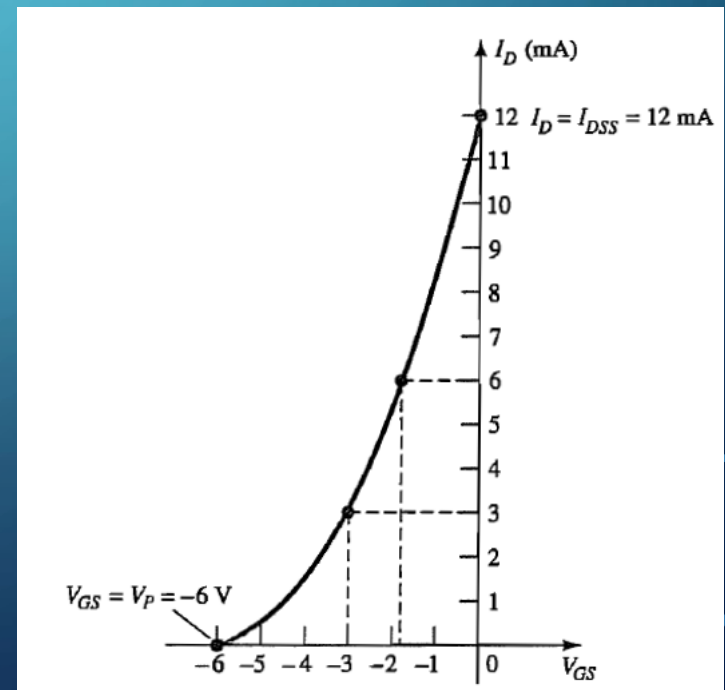

FET BIASING (SELF BIAS CONFIGURATION)

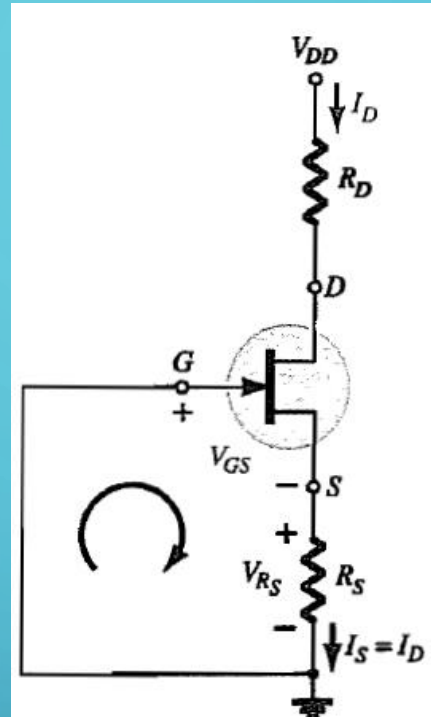

For the dc analysis, the capacitors can again be replaced by “open circuits” and the resistor R_G replaced by a short-circuit equivalent since $I_G = 0$ A. The result is the network of Fig. 7.9 for the important dc analysis.

The current through R_S is the source current I_S , but $I_S = I_D$ and

$$V_{R_S} = I_D R_S$$

For the indicated closed loop of Fig. 7.9, we find that

$$-V_{GS} - V_{R_S} = 0$$


and

$$V_{GS} = -V_{R_S}$$

or

$$V_{GS} = -I_D R_S$$

(7.10)

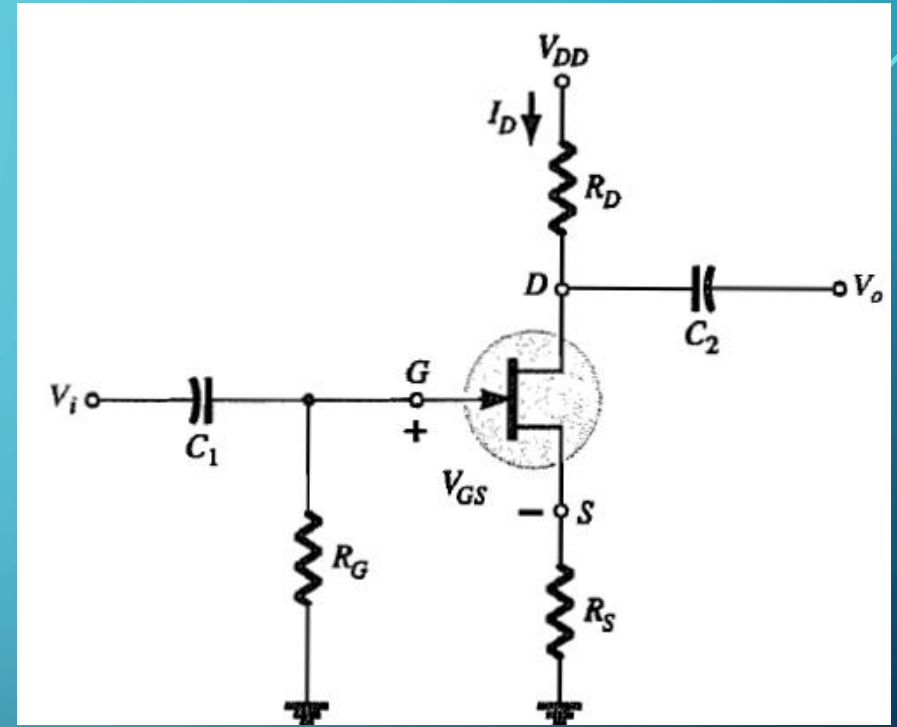

FET BIASING (SELF BIAS CONFIGURATION)


$$I_D = I_S$$

$$V_{DS} = V_{DD} - I_D(R_S + R_D)$$

$$V_S = I_D R_S$$

$$V_G = 0 \text{ V}$$
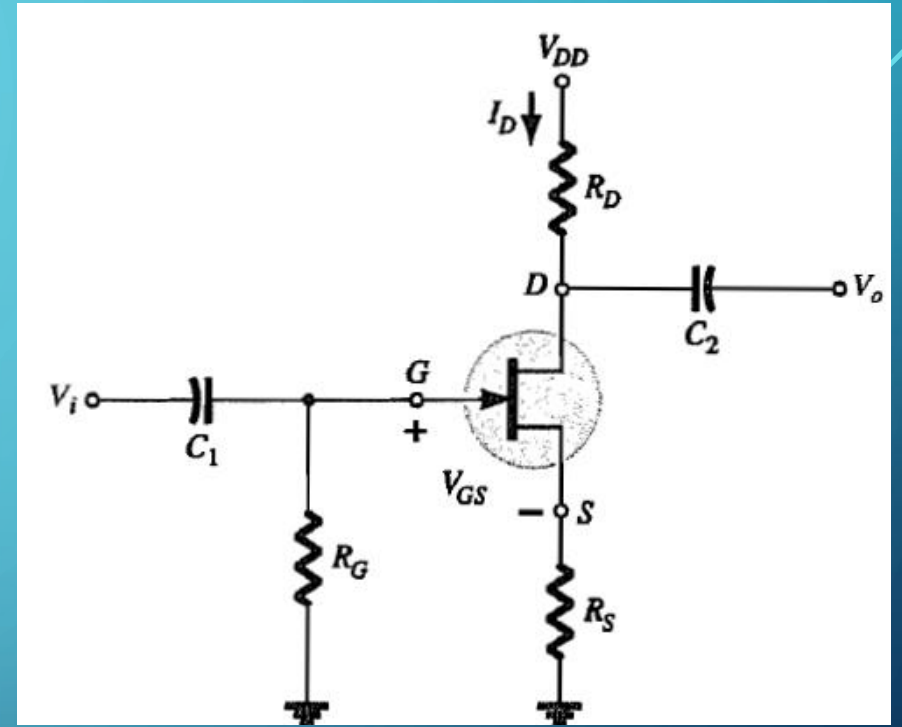
$$V_D = V_{DS} + V_S = V_{DD} - V_{R_D}$$



FET BIASING (SELF BIAS CONFIGURATION)

a. The gate-to-source voltage is determined by

$$V_{GS} = -I_D R_S$$

Choosing $I_D = 4 \text{ mA}$, we obtain

$$V_{GS} = -(4 \text{ mA})(1 \text{ k}\Omega) = -4 \text{ V}$$

The result is the plot of Fig. 7.13 as defined by the network.

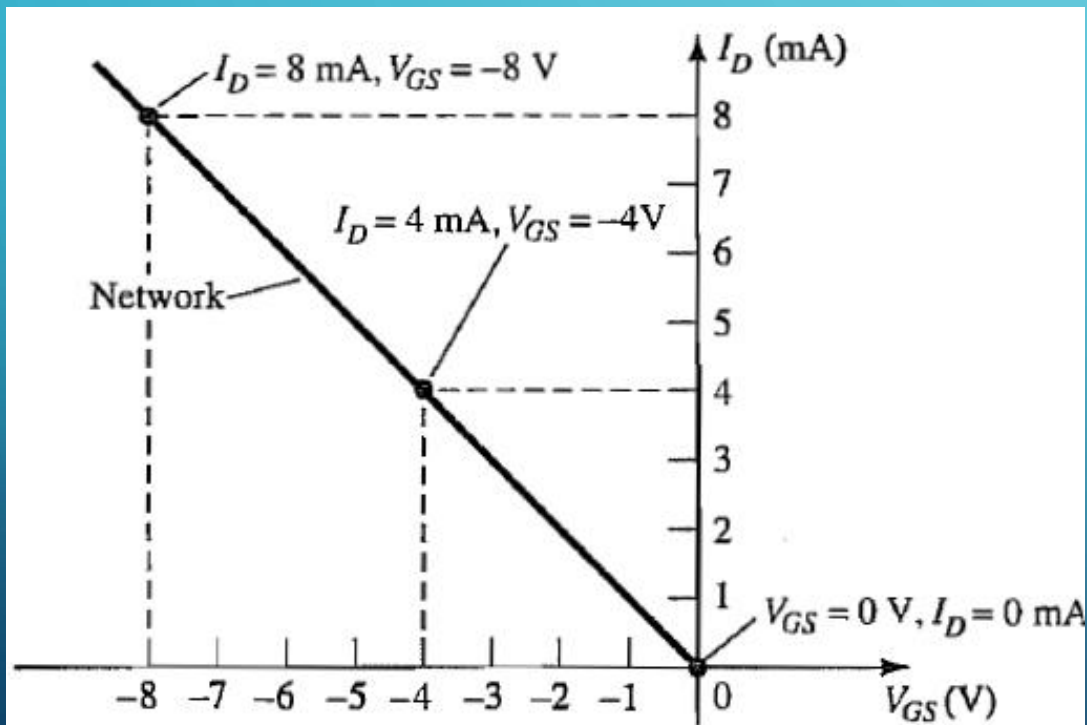


FIG. 7.13

EXAMPLE 7.2 Determine the following for the network of Fig. 7.12:

- V_{GSQ}
- I_{DQ}
- V_{DS}
- V_S
- V_G
- V_D

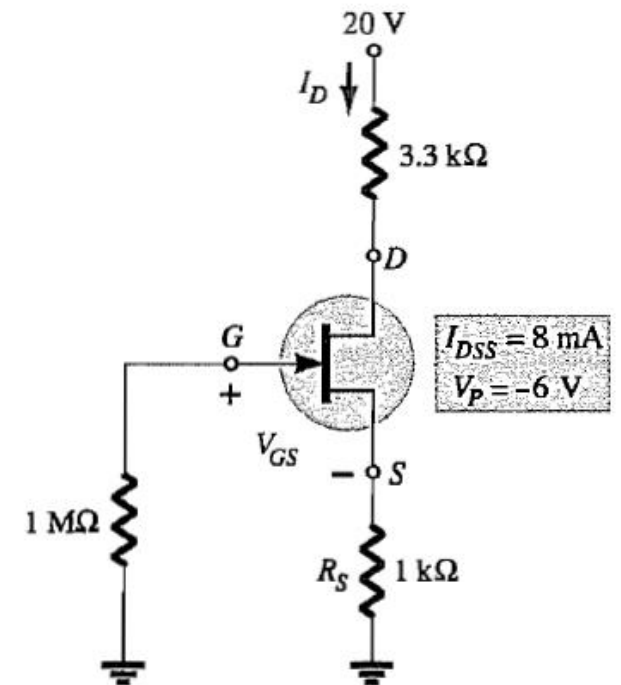


FIG. 7.12

FET BIASING (SELF BIAS CONFIGURATION)

$$V_{GSQ} = -2.6 \text{ V}$$

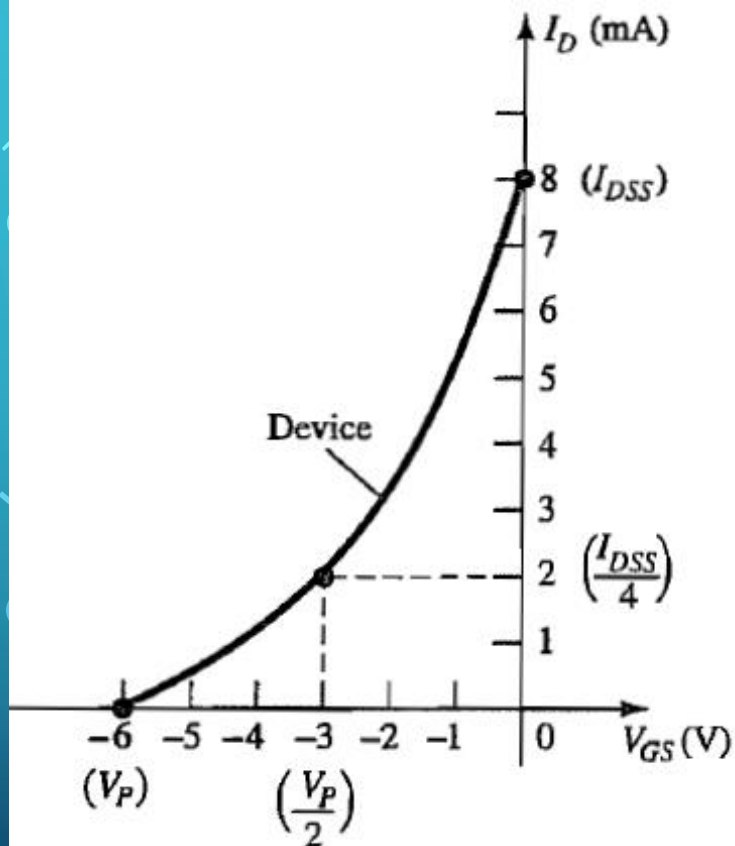


FIG. 7.14

Sketching the device characteristics for the JFET of Fig. 7.12.

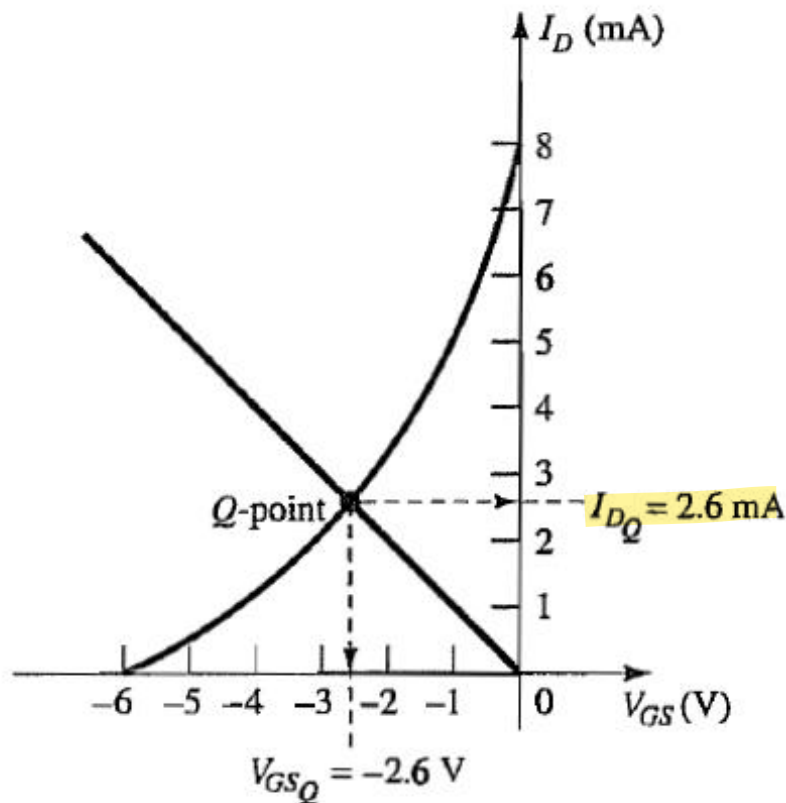


FIG. 7.15

Determining the Q -point for the network of Fig. 7.12.

EXAMPLE 7.2 Determine the following for the network of Fig. 7.12:

- V_{GSQ}
- I_{DQ}
- V_{DS}
- V_S
- V_G
- V_D

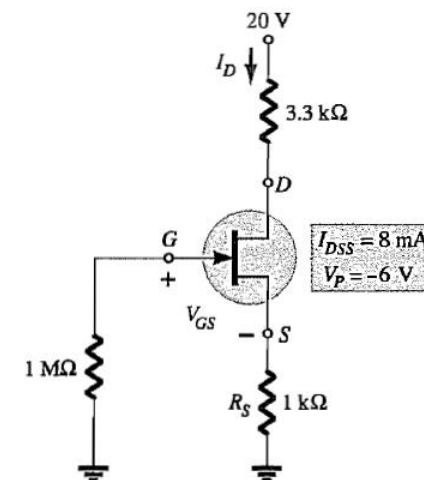


FIG. 7.12

b. At the quiescent point

$$I_{DQ} = 2.6 \text{ mA}$$

c. Eq. (7.11): $V_{DS} = V_{DD} - I_D(R_S + R_D)$
 $= 20 \text{ V} - (2.6 \text{ mA})(1 \text{ k}\Omega + 3.3 \text{ k}\Omega)$
 $= 20 \text{ V} - 11.18 \text{ V}$
 $= 8.82 \text{ V}$

d. Eq. (7.12): $V_S = I_D R_S$
 $= (2.6 \text{ mA})(1 \text{ k}\Omega)$
 $= 2.6 \text{ V}$

e. Eq. (7.13): $V_G = 0 \text{ V}$

f. Eq. (7.14): $V_D = V_{DS} + V_S = 8.82 \text{ V} + 2.6 \text{ V} = 11.42 \text{ V}$
 or $V_D = V_{DD} - I_D R_D = 20 \text{ V} - (2.6 \text{ mA})(3.3 \text{ k}\Omega) = 11.42 \text{ V}$

FET BIASING (FIXED BIAS CONFIGURATION)

$$I_G \cong 0 \text{ A}$$
$$V_{R_G} = I_G R_G = (0 \text{ A}) R_G = 0 \text{ V}$$

$$-V_{GG} - V_{GS} = 0$$

$$V_{GS} = -V_{GG}$$


$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$+V_{DS} + I_D R_D - V_{DD} = 0$$

$$V_{DS} = V_{DD} - I_D R_D$$

$$V_S = 0 \text{ V}$$

JFET		BJT
$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$	\Leftrightarrow	$I_C = \beta I_B$
$I_D = I_S$	\Leftrightarrow	$I_C \cong I_E$
$I_G \cong 0 \text{ A}$	\Leftrightarrow	$V_{BE} \cong 0.7 \text{ V}$

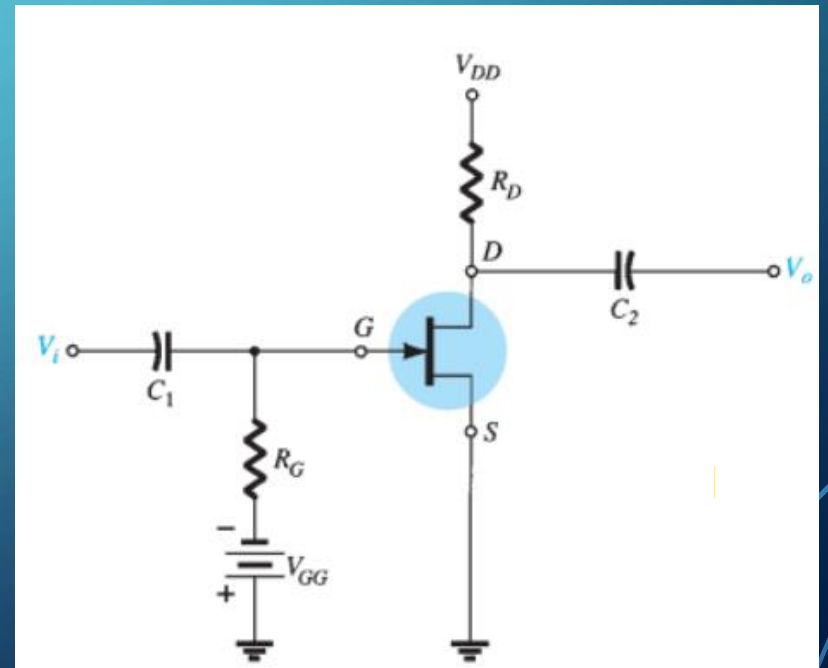

FET BIASING (FIXED BIAS CONFIGURATION)

$$V_{DS} = V_D - V_S$$


$$V_D = V_{DS} + V_S = V_{DS} + 0 \text{ V}$$

$$V_D = V_{DS}$$

$$V_{GS} = V_G - V_S$$

$$V_G = V_{GS} + V_S = V_{GS} + 0 \text{ V}$$

$$V_G = V_{GS}$$

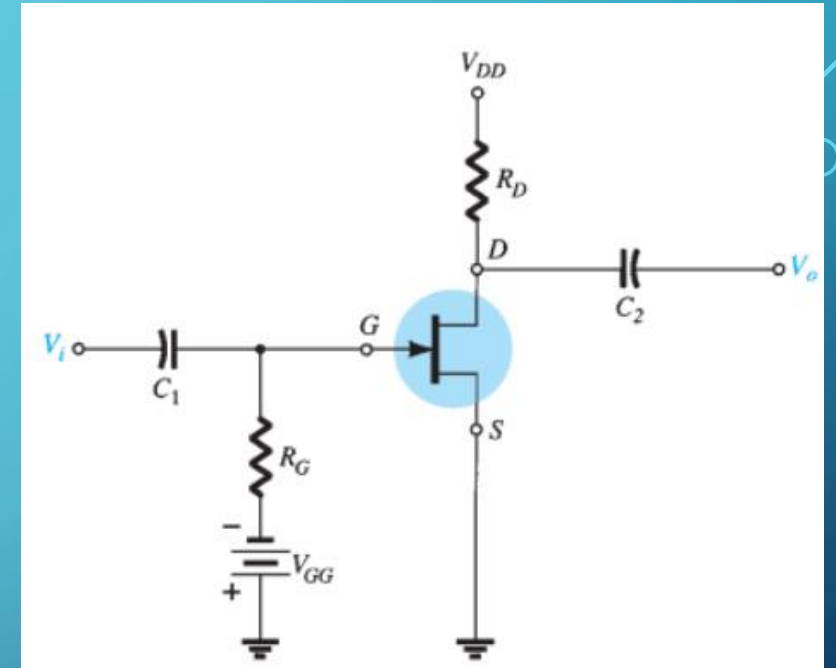

FET BIASING (FIXED BIAS CONFIGURATION)

EXAMPLE 7.1 Determine the following for the network of Fig. 7.6:

- a. V_{GS_Q}
- b. I_{D_Q}
- c. V_{DS}
- d. V_D
- e. V_G
- f. V_S

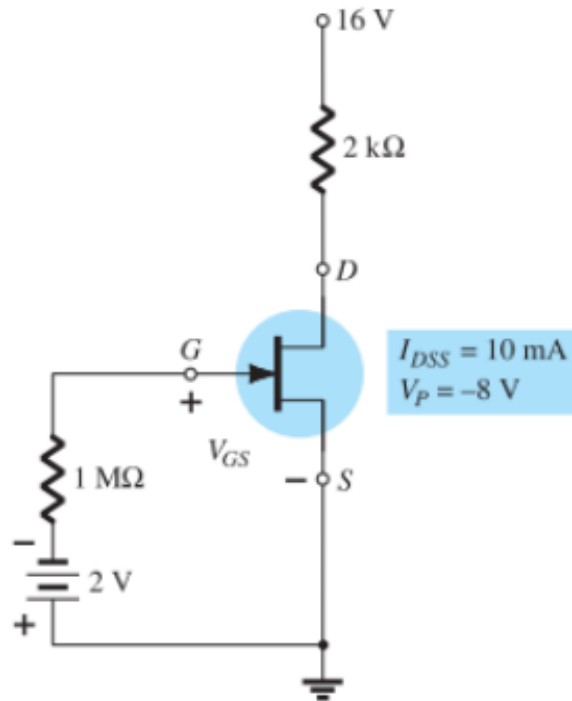



FIG. 7.6

Example 7.1.

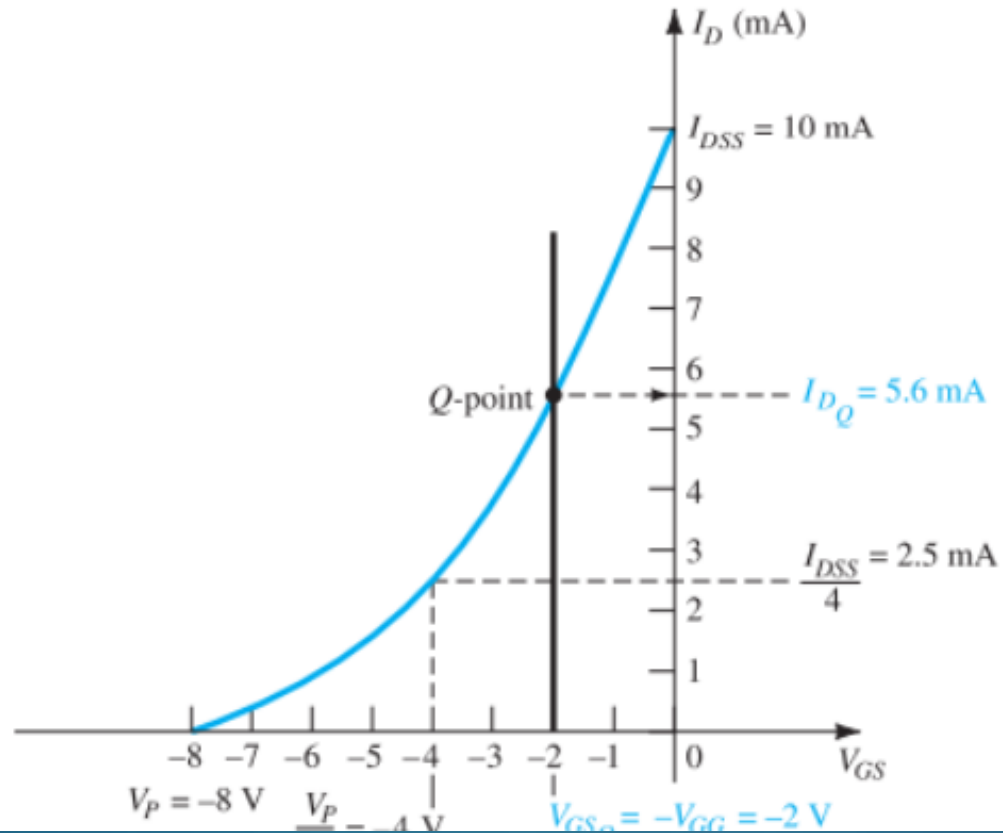- a. $V_{GS_Q} = -V_{GG} = -2 \text{ V}$
- b.
$$I_{D_Q} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = 10 \text{ mA} \left(1 - \frac{-2 \text{ V}}{-8 \text{ V}} \right)^2$$
$$= 10 \text{ mA} (1 - 0.25)^2 = 10 \text{ mA} (0.75)^2 = 10 \text{ mA} (0.5625)$$
$$= \mathbf{5.625 \text{ mA}}$$
- c.
$$V_{DS} = V_{DD} - I_D R_D = 16 \text{ V} - (5.625 \text{ mA})(2 \text{ k}\Omega)$$
$$= 16 \text{ V} - 11.25 \text{ V} = \mathbf{4.75 \text{ V}}$$
- d. $V_D = V_{DS} = \mathbf{4.75 \text{ V}}$
- e. $V_G = V_{GS} = -2 \text{ V}$
- f. $V_S = \mathbf{0 \text{ V}}$

FET BIASING (FIXED BIAS CONFIGURATION)

Graphical Approach The resulting Shockley curve and the vertical line at $V_{GS} = -2\text{ V}$ are provided in Fig. 7.7. It is certainly difficult to read beyond the second place without



significantly increasing the size of the figure, but a solution of 5.6 mA from the graph of Fig. 7.7 is quite acceptable.

FET BIASING (FIXED BIAS CONFIGURATION)

a. Therefore,

$$V_{GS_Q} = -V_{GG} = -2 \text{ V}$$

b. $I_{D_Q} = 5.6 \text{ mA}$


c. $V_{DS} = V_{DD} - I_D R_D = 16 \text{ V} - (5.6 \text{ mA})(2 \text{ k}\Omega)$
 $= 16 \text{ V} - 11.2 \text{ V} = 4.8 \text{ V}$

d. $V_D = V_{DS} = 4.8 \text{ V}$

e. $V_G = V_{GS} = -2 \text{ V}$

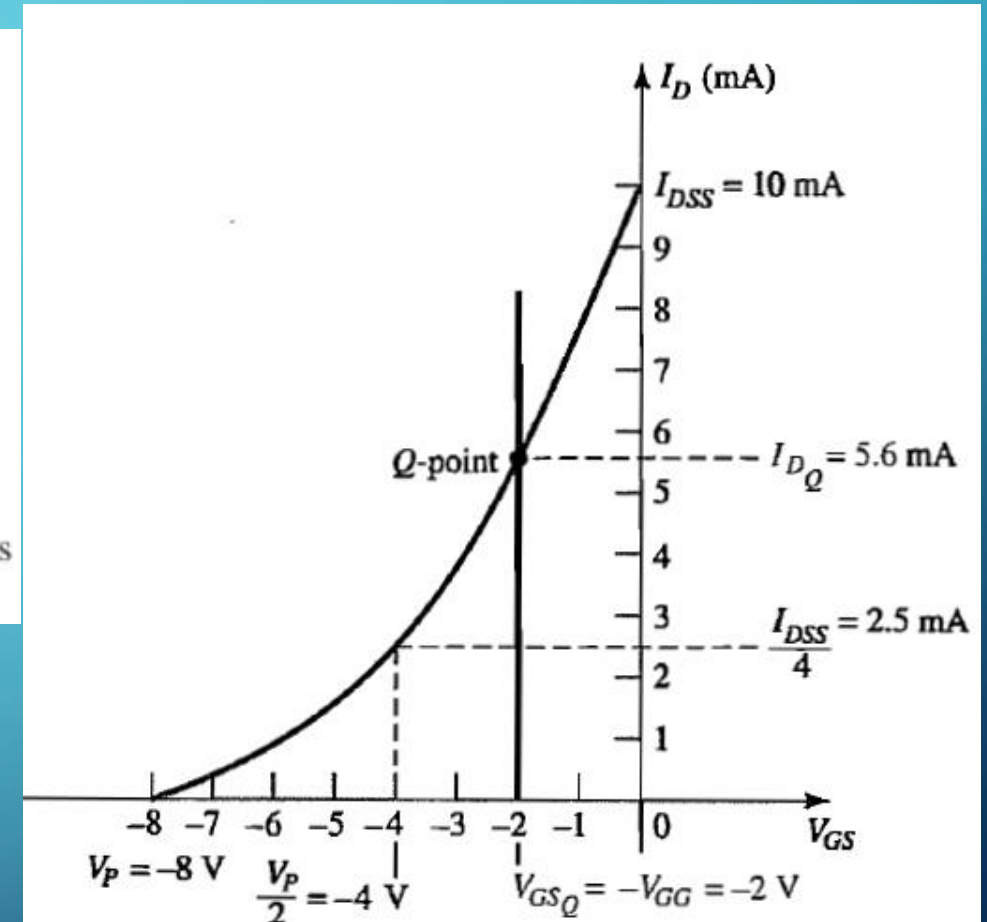f. $V_S = 0 \text{ V}$

The results clearly confirm the fact that the mathematical and graphical approaches generate solutions that are quite close.



FET BIASING (VOLTAGE DIVIDER BIAS CONFIGURATION)

$$I_G \cong 0 \text{ A}$$

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$V_G - V_{GS} - V_{R_S} = 0$$
$$V_{GS} = V_G - V_{R_S}$$

$$V_{GS} = V_G - I_D R_S$$

$$V_{GS} = V_G - I_D R_S$$
$$= V_G - (0 \text{ mA}) R_S$$

$$V_{GS} = V_G |_{I_D=0 \text{ mA}}$$

$$V_{GS} = V_G - I_D R_S$$
$$0 \text{ V} = V_G - I_D R_S$$


$$I_D = \frac{V_G}{R_S} \Big|_{V_{GS}=0 \text{ V}}$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$


$$V_D = V_{DD} - I_D R_D$$

$$V_S = I_D R_S$$
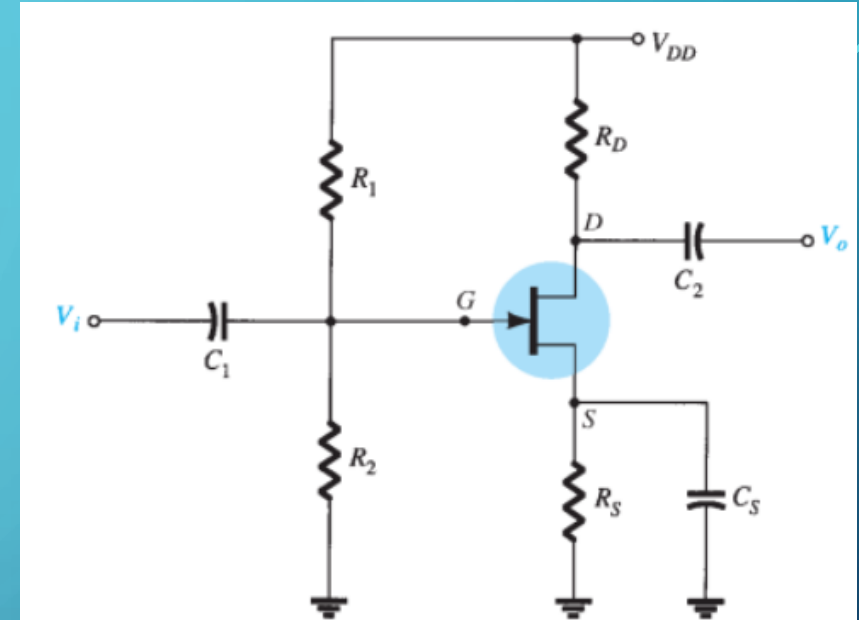
$$I_{R_1} = I_{R_2} = \frac{V_{DD}}{R_1 + R_2}$$



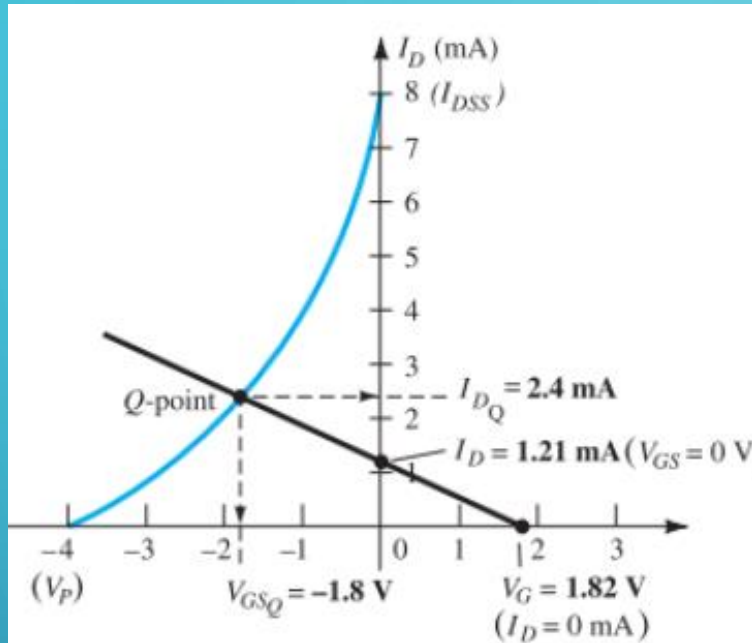FET BIASING (VOLTAGE DIVIDER BIAS CONFIGURATION)



- a. For the transfer characteristics, if $I_D = I_{DSS}/4 = 8 \text{ mA}/4 = 2 \text{ mA}$, then $V_{GS} = V_P/2 = -4 \text{ V}/2 = -2 \text{ V}$. The resulting curve representing Shockley's equation appears in Fig. 7.22. The network equation is defined by

$$\begin{aligned} V_G &= \frac{R_2 V_{DD}}{R_1 + R_2} \\ &= \frac{(270 \text{ k}\Omega)(16 \text{ V})}{2.1 \text{ M}\Omega + 0.27 \text{ M}\Omega} \\ &= 1.82 \text{ V} \end{aligned}$$

and

$$\begin{aligned} V_{GS} &= V_G - I_D R_S \\ &= 1.82 \text{ V} - I_D (1.5 \text{ k}\Omega) \end{aligned}$$

EXAMPLE 7.4 Determine the following for the network of Fig. 7.21:

- I_{D_Q} and V_{GS_Q} .
- V_D .
- V_S .
- V_{DS} .
- V_{DG} .

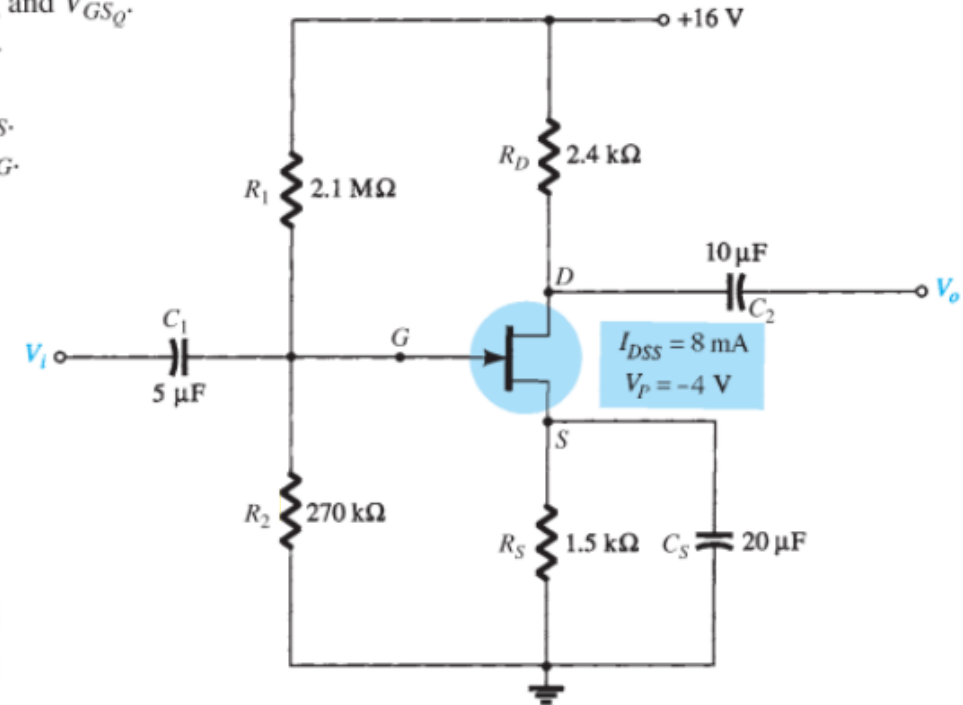


FIG. 7.21

Example 7.4.

FET BIASING (VOLTAGE DIVIDER BIAS CONFIGURATION)

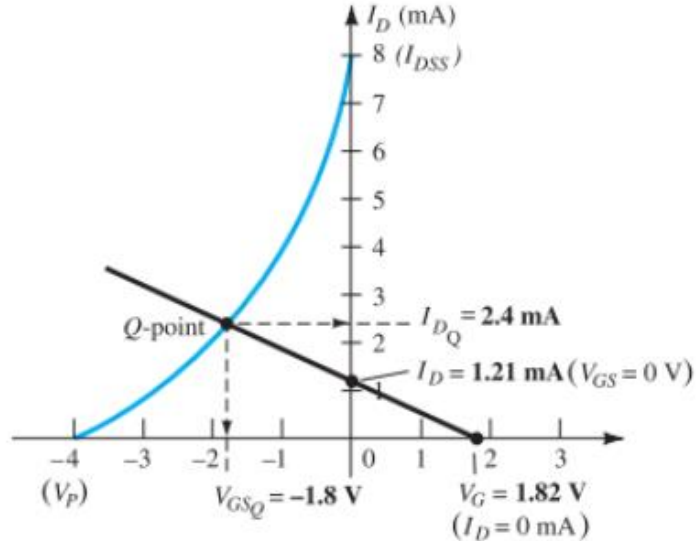


FIG. 7.22

Determining the Q-point for the network of Fig. 7.21.

When $I_D = 0$ mA,

$$V_{GS} = +1.82 \text{ V}$$

When $V_{GS} = 0$ V,

$$I_D = \frac{1.82 \text{ V}}{1.5 \text{ k}\Omega} = 1.21 \text{ mA}$$

The resulting bias line appears on Fig. 7.22 with quiescent values of

$$I_{DQ} = 2.4 \text{ mA}$$

$$V_{GSQ} = -1.8 \text{ V}$$

$$\begin{aligned} \text{b. } V_D &= V_{DD} - I_D R_D \\ &= 16 \text{ V} - (2.4 \text{ mA})(2.4 \text{ k}\Omega) \\ &= 10.24 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{c. } V_S &= I_D R_S = (2.4 \text{ mA})(1.5 \text{ k}\Omega) \\ &= 3.6 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{d. } V_{DS} &= V_{DD} - I_D(R_D + R_S) \\ &= 16 \text{ V} - (2.4 \text{ mA})(2.4 \text{ k}\Omega + 1.5 \text{ k}\Omega) \\ &= 6.64 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{or } V_{DS} &= V_D - V_S = 10.24 \text{ V} - 3.6 \text{ V} \\ &= 6.64 \text{ V} \end{aligned}$$

EXAMPLE 7.4 Determine the following for the network of Fig. 7.21:

- I_{DQ} and V_{GSQ} .
- V_D .
- V_S .
- V_{DS} .
- V_{DG} .

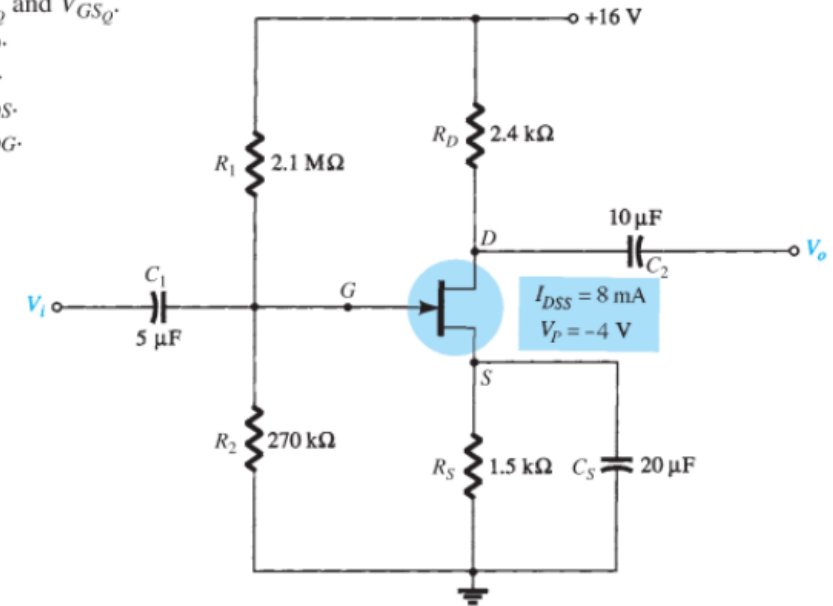


FIG. 7.21
Example 7.4.

e. Although seldom requested, the voltage V_{DG} can easily be determined using

$$\begin{aligned} V_{DG} &= V_D - V_G \\ &= 10.24 \text{ V} - 1.82 \text{ V} \\ &= 8.42 \text{ V} \end{aligned}$$

The background is a blue gradient with faint concentric circles. White circuit-like lines with circular nodes are positioned in the corners: top-left, top-right, bottom-left, and bottom-right.

Thank You!