
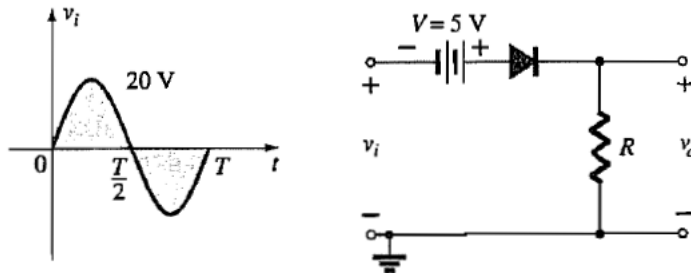


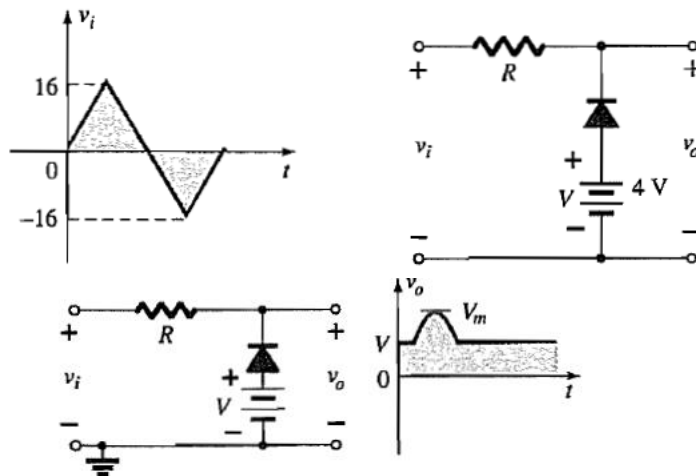
1. Determine the output waveshape of the following circuit




2. Determine V_o for the following circuit



- 3.

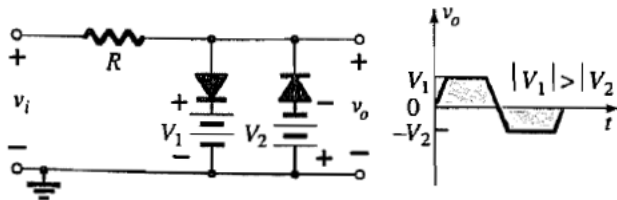

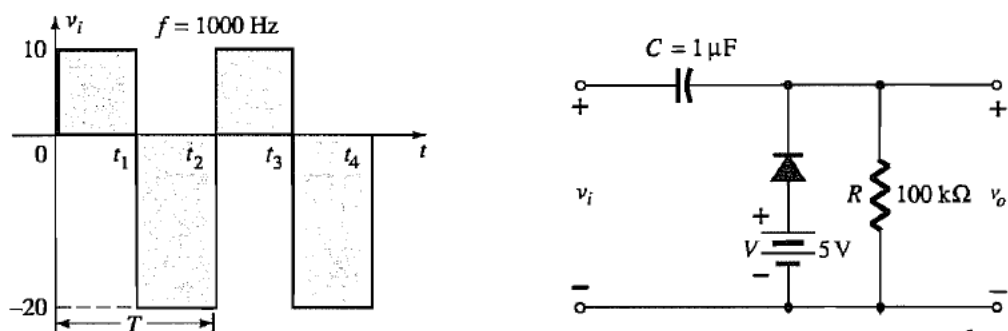- 4.
5. Determine V_o for the given network



6.

