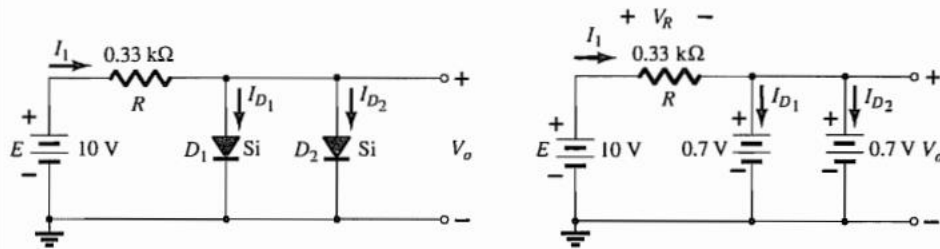



1.

Determine V_o , I_1 , I_{D_1} , and I_{D_2} for the parallel diode configuration of Fig.



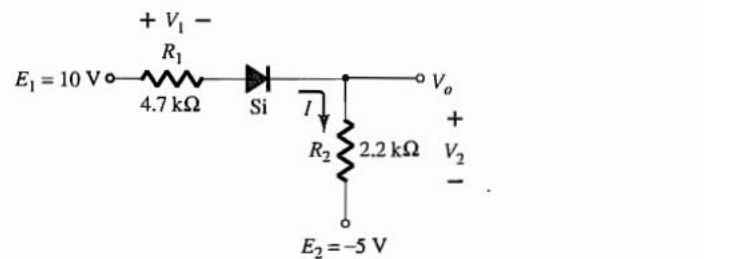
2.

Determine I , V_1 , V_2 , and V_o for the series dc configuration of Fig.




3.

Determine V_o for the network of Fig.

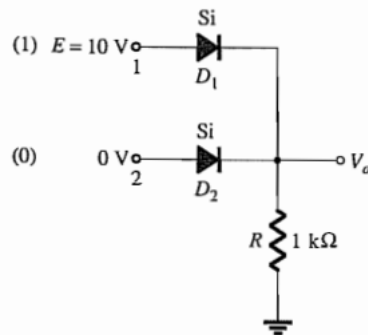


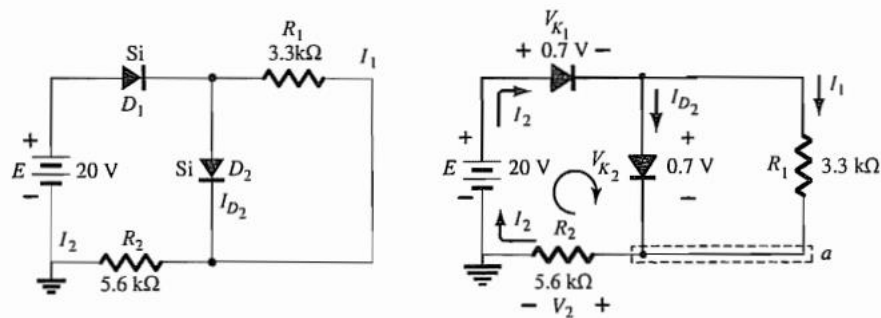
4.

Determine the currents I_1 , I_2 , and I_{D_2} for the network of Fig.



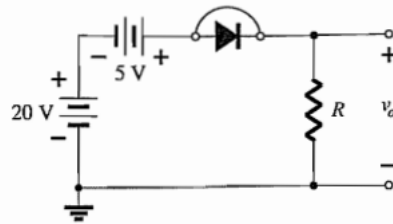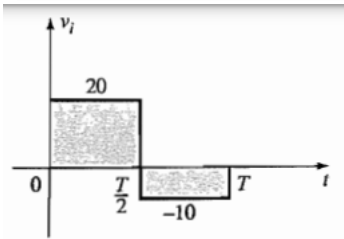5.

Find the output voltage for the network examined in Example 1.1 if the applied signal is the square wave of Fig. .



6. For a semiconductor diode, if forward current is 10mA at $V_d = 0.3$ V, then what is the forward current at $V_d = 0.4$ V. Ans: 545.98 mA.
7. If diode current made twice and $V_T = 25$ mV, then find the voltage increase in the diode. Ans: 17.325 mV